

Figure 3-1 Basic ROM Structure

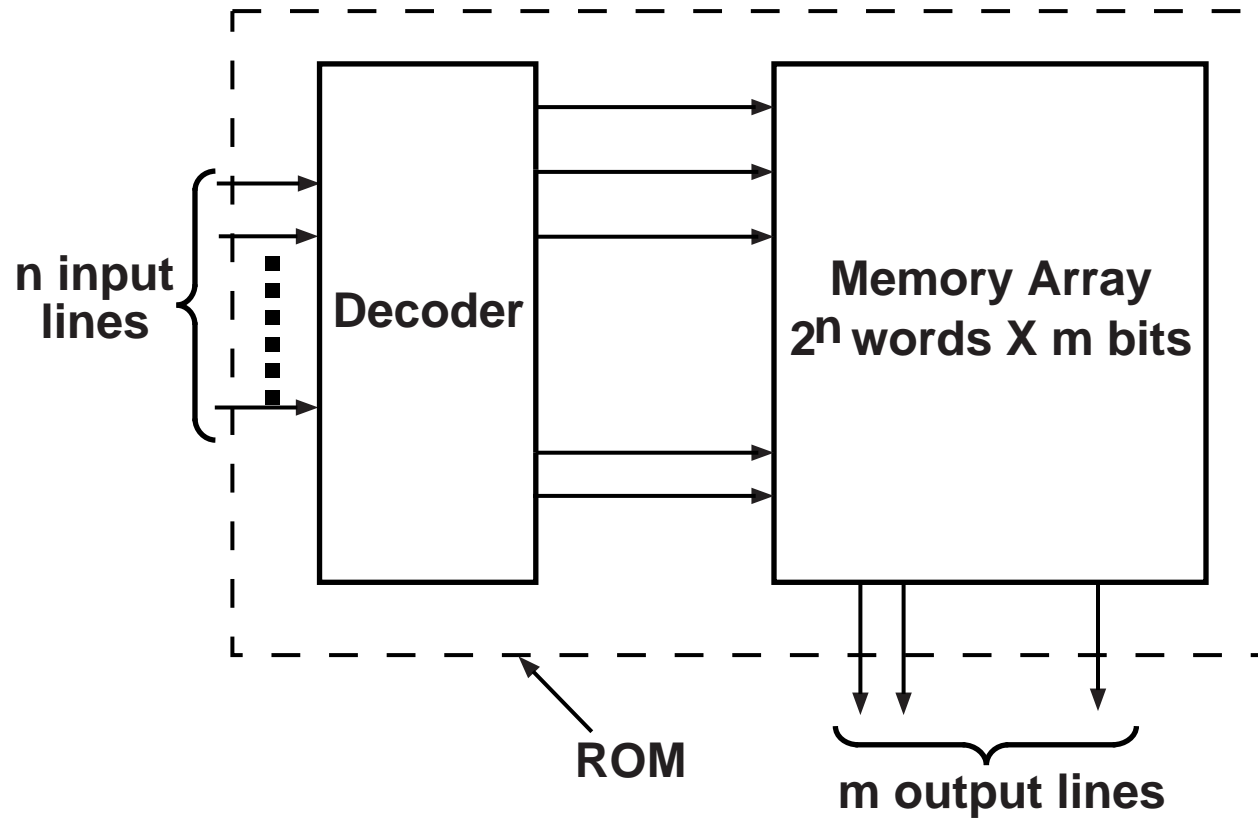


Figure 3-2
Realization of a Mealy Sequential Network with a ROM

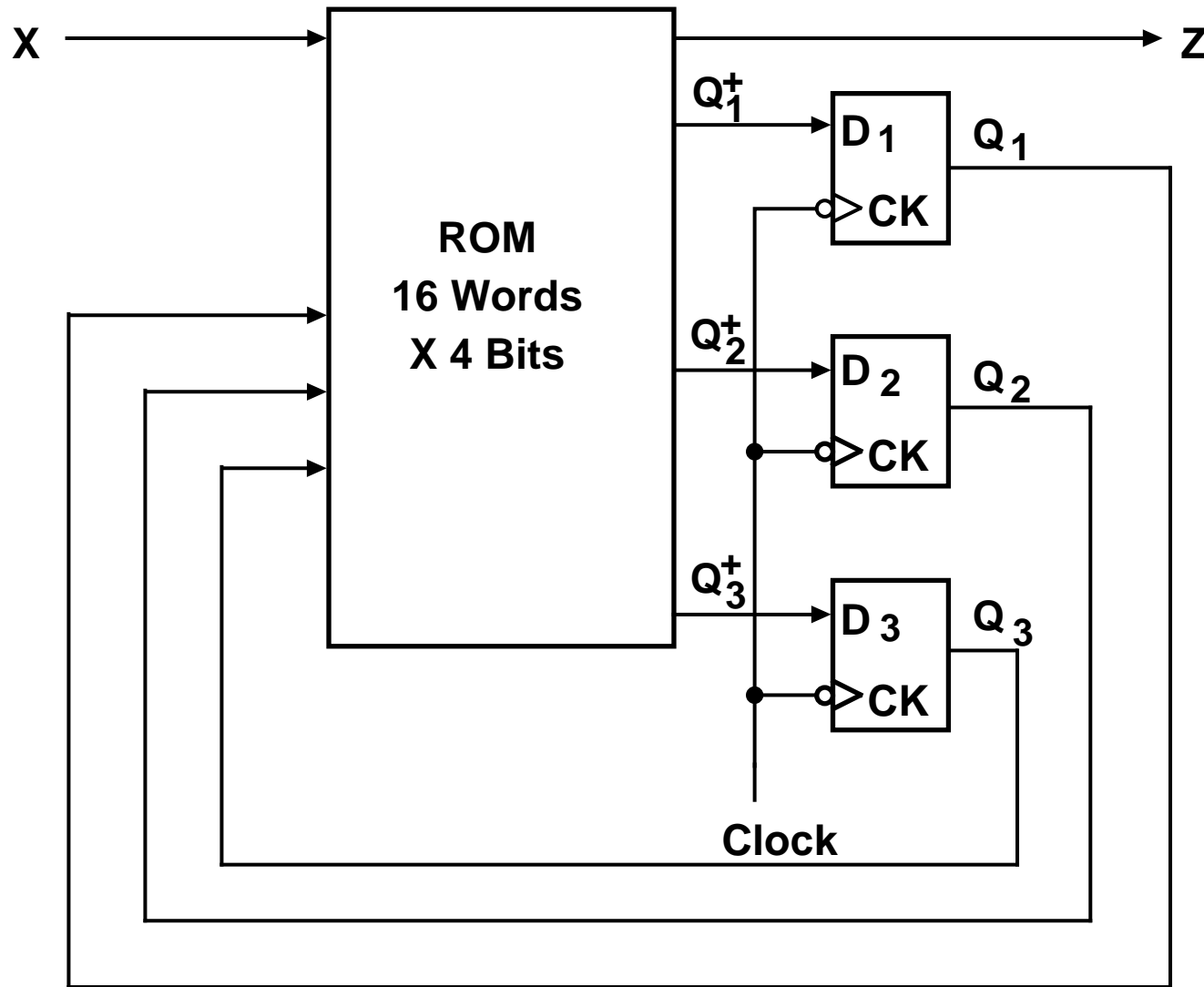


Table 3-1 ROM Truth Table

Q1	Q2	Q3	X	Q1 ⁺	Q2 ⁺	Q3 ⁺	Z
0	0	0	0	1	0	0	1
0	0	0	1	1	0	1	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	0	0
0	1	1	0	0	0	0	0
0	1	1	1	0	0	0	1
1	0	0	0	1	1	1	1
1	0	0	1	1	1	0	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	0	1	1	1
1	1	0	1	0	1	0	0
1	1	1	0	0	1	1	0
1	1	1	1	0	1	1	1

Q1	Q2	Q3	Q1 ⁺ Q2 ⁺ Q3 ⁺		Z	
			X=0	1	X=0	1
000	100	101	1	0		
100	111	110	1	0		
101	110	110	0	1		
111	011	011	0	1		
110	011	010	1	0		
011	000	000	0	1		
010	000	xxx	1	x		
001	xxx	xxx	x	x		

Figure 3-3 ROM Realization of Figure 1-17

```
library BITLIB;
use BITLIB.bit_pack.all;

entity ROM1_2 is
    port(X,CLK: in bit;
         Z: out bit);
end ROM1_2;

architecture ROM1 of ROM1_2 is
    signal Q, Qplus: bit_vector(1 to 3) := "000";
    type ROM is array (0 to 15) of bit_vector(3 downto 0);
    constant FSM_ROM: ROM :=
        ("1001","1010","0000","0000","0001","0000","0000","0001",
         "1111","1100","1100","1101","0111","0100","0110","0111");
begin
    process(Q,X) -- determines the next state and output
        variable ROMValue: bit_vector(3 downto 0);
    begin
        ROMValue := FSM_ROM(vec2int(Q & X)); -- read ROM output
        Qplus <= ROMValue(3 downto 1);
        Z <= ROMValue(0);
    end process;

    process(CLK)
    begin
        if CLK='1' then Q <= Qplus; end if; -- update state register
    end process;
end ROM1;
```

Figure 3-4 Programmable Logic Array Structure

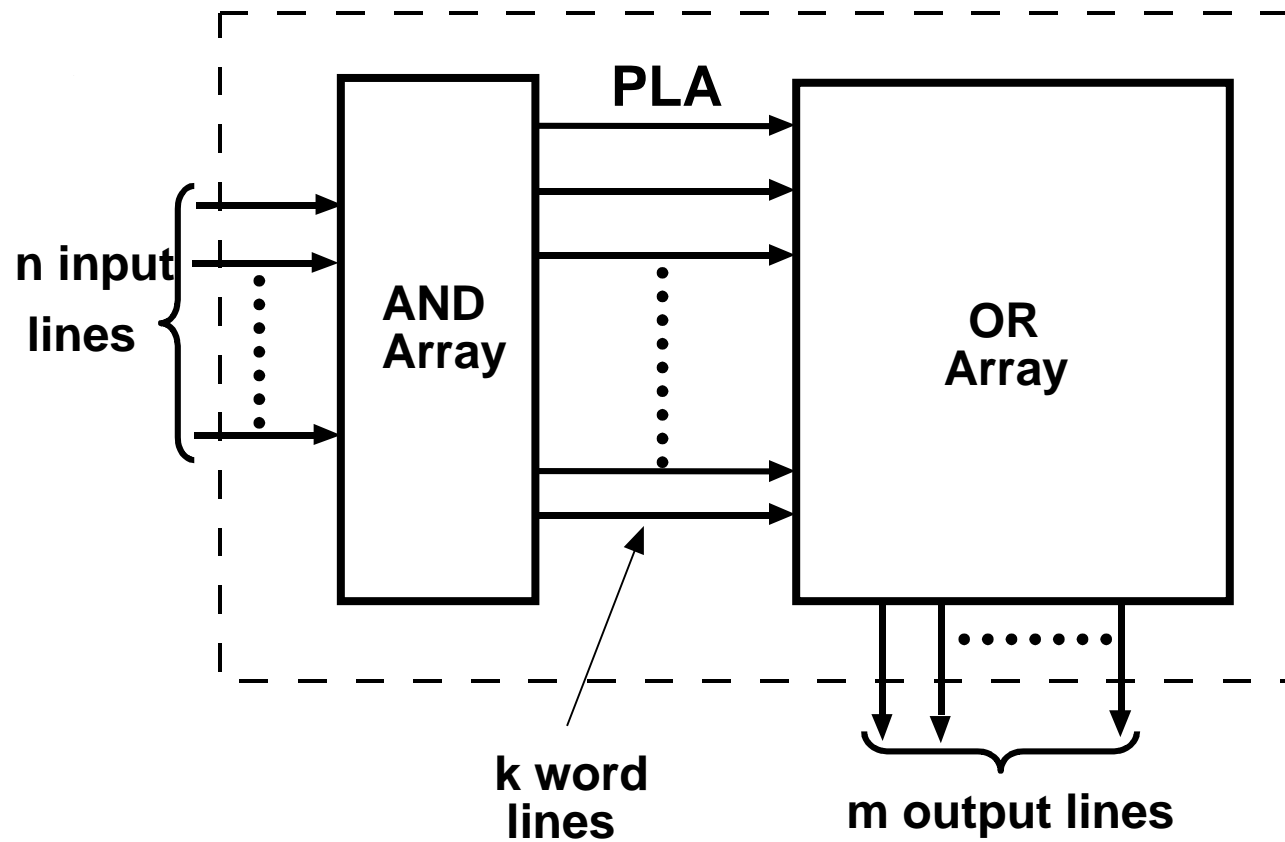


Figure 3-5 PLA with 3 input, 5 Product Terms, and 4 Outputs

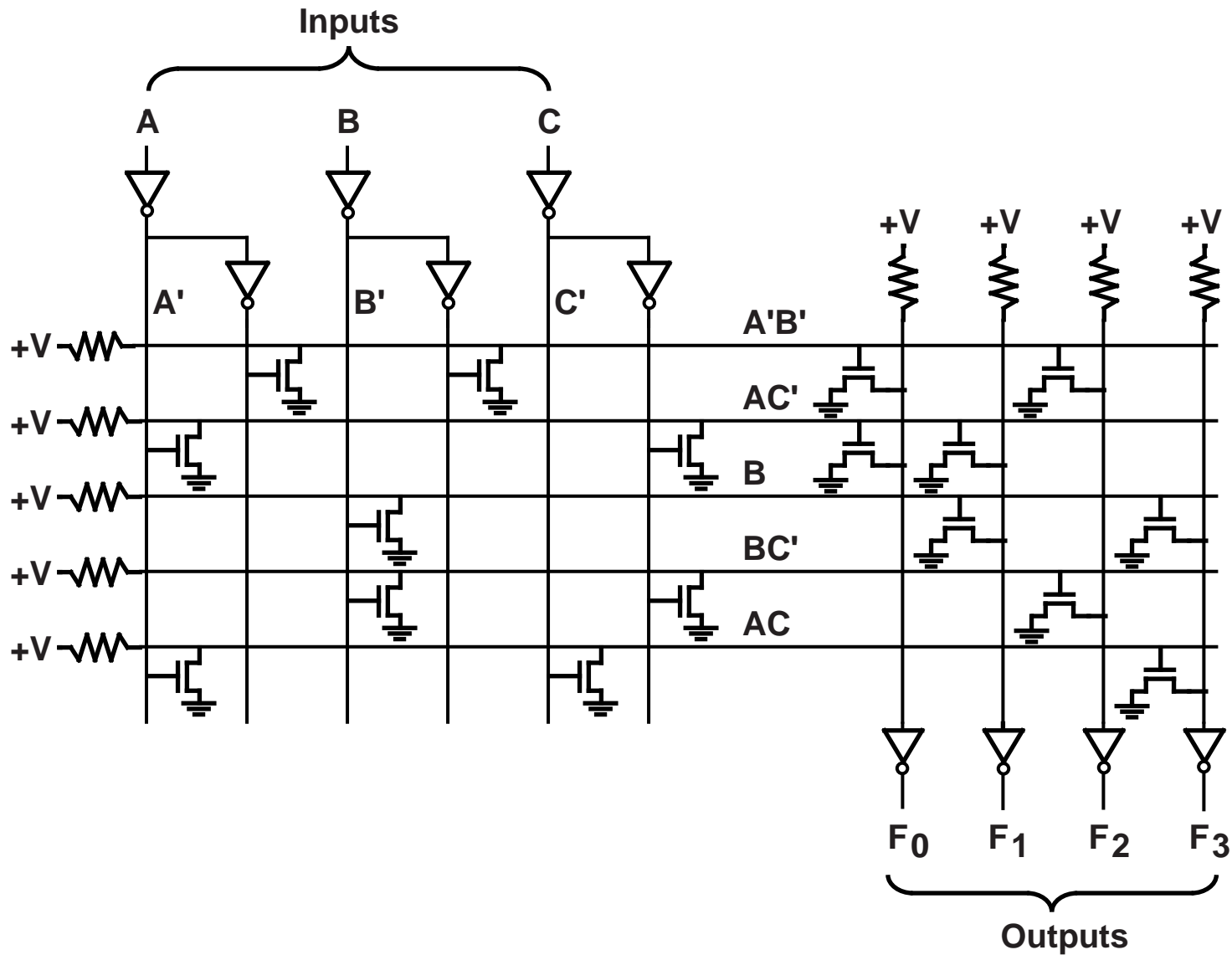


Figure 3-6 nMOS NOR Gate

 


Figure 3-7 Conversion for NOR-NOR to AND-OR

 


Figure 3-8 AND-OR Array Equivalent to Figure 3-5


 


Table 3-2 PLA Table for Figure 3-5

Product	Inputs			Outputs			
	A	B	C	F0	F1	F2	F3
A'B'	0	0	-	1	0	1	0
AC'	1	-	0	1	1	0	0
B	-	1	-	0	1	0	1
BC'	-	1	0	0	0	1	0
AC	1	-	1	0	0	0	1

Figure 3-9 Multiple Output Karnaugh Maps

 

a	b	c	d	F1	F2	F3
0	1	-	1	1	1	0
1	1	-	1	1	0	1
1	0	0	-	1	0	1
-	0	1	-	1	1	0
-	1	1	-	0	1	1

$$F1 = a'bd + abd + ab'c' + b'c$$

$$F2 = a'bd + b'c + bc$$

$$F3 = abd + ab'c' + bc$$

Table 3-3 Reduced PLA Table

a	b	c	d	F ₁	F ₂	F ₃
0	1	–	1	1	1	0
1	1	–	1	1	0	1
1	0	0	–	1	0	1
–	0	1	–	1	1	0
–	1	1	–	0	1	1

$$F_1 = a'bd + abd + ab'c' + b'c$$

$$F_2 = a'bd + b'c + bc$$

$$F_3 = abd + ab'c' + bc$$

Figure 3-10 PLA Realization of Equations

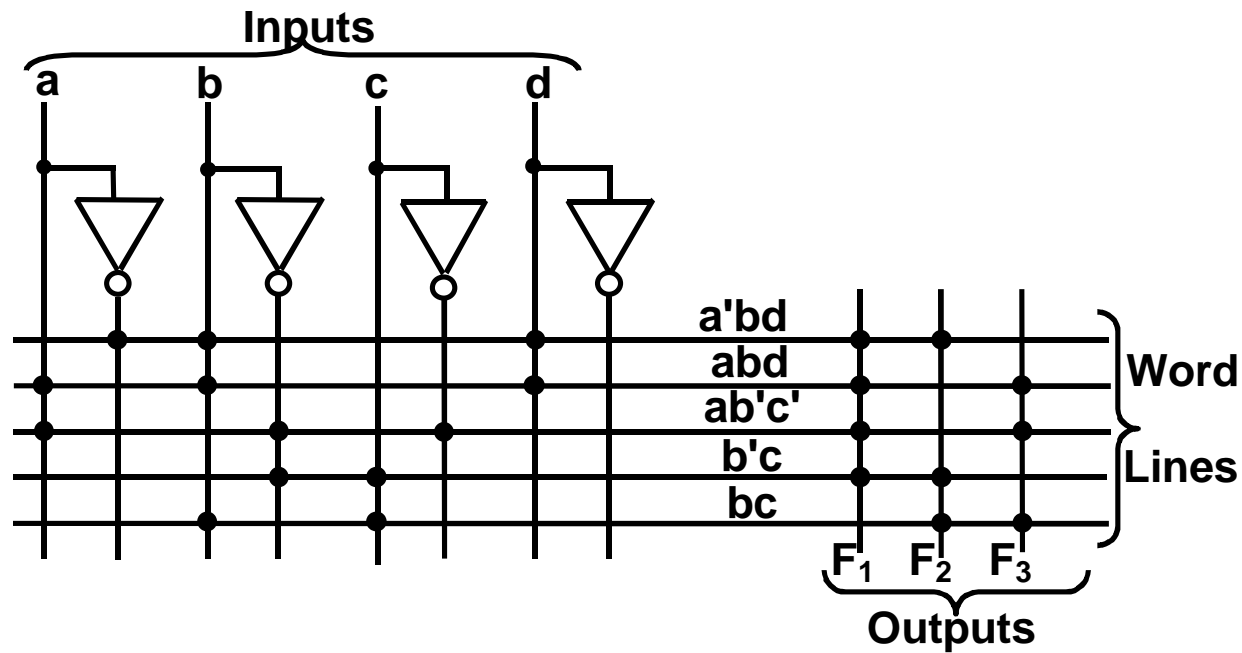


Table 3-4 PLA Table (Based on Figures 1-17 and 1-19)

Product Term	Q1	Q2	Q3	X	Q1 ⁺	Q2 ⁺	Q3 ⁺	Z
Q2'	–	0	–	–	1	0	0	0
Q1	1	–	–	–	0	1	0	0
Q1Q2Q3	1	1	1	–	0	0	1	0
Q1Q3'X'	1	–	0	0	0	0	1	0
Q1'Q2'X	0	0	–	1	0	0	1	0
Q3'X'	–	–	0	0	0	0	0	1
Q3X	–	–	1	1	0	0	0	1

$$Q1^+ = Q2'$$

$$Q2^+ = Q1$$

$$Q3^+ = Q1Q2Q3 + X'Q1Q3' + XQ1'Q2'$$

$$Z = X'Q3' + XQ3$$

Figure 3-11 PLA Realization of Figure 1-17

```
library ieee;
use ieee.std_logic_1164.all;           -- IEEE standard logic package
library MVLlib;                       -- includes PLAmtrx type and
use MVLlib.mvl_pack.all;             -- PLAout function


entity PLA1_2 is
    port(X,CLK: in std_logic;
          Z: out std_logic);
end PLA1_2;

architecture PLA of PLA1_2 is
signal Q, Qplus: std_logic_vector(1 to 3) := "000";
constant FSM_PLA: PLAmtrx(0 to 6, 7 downto 0) :=
    ("X0XX1000","1XXX0100","111X0010","1X000010",
     "00X10010","XX000001","XX110001");


begin
    process(Q,X)
        variable PLAValue: std_logic_vector(3 downto 0);
        begin
            PLAValue := PLAout(FSM_PLA,Q & X);           -- read PLA output
            Qplus <= PLAValue(3 downto 1);
            Z <= PLAValue(0);
        end process;

        process(CLK)
            begin
                if CLK='1' then Q <= Qplus; end if;           -- update state register
            end process;
end PLA;
```

Figure 3-12 Combinational PAL Segment

 

(a) Unprogrammed

 

(b) Programmed

Figure 3-13 Segment of a Sequential PAL

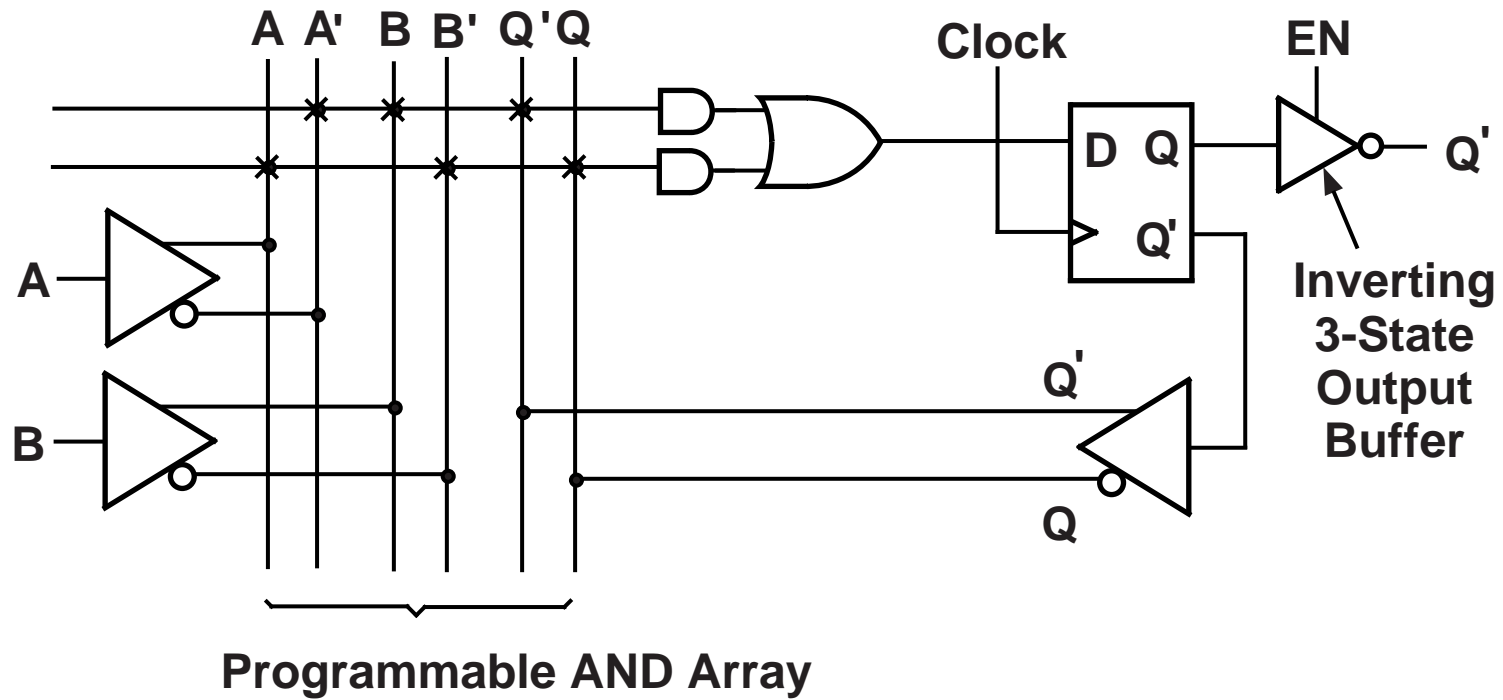


Figure 3-14a Logic Diagram for 16R4 PAL

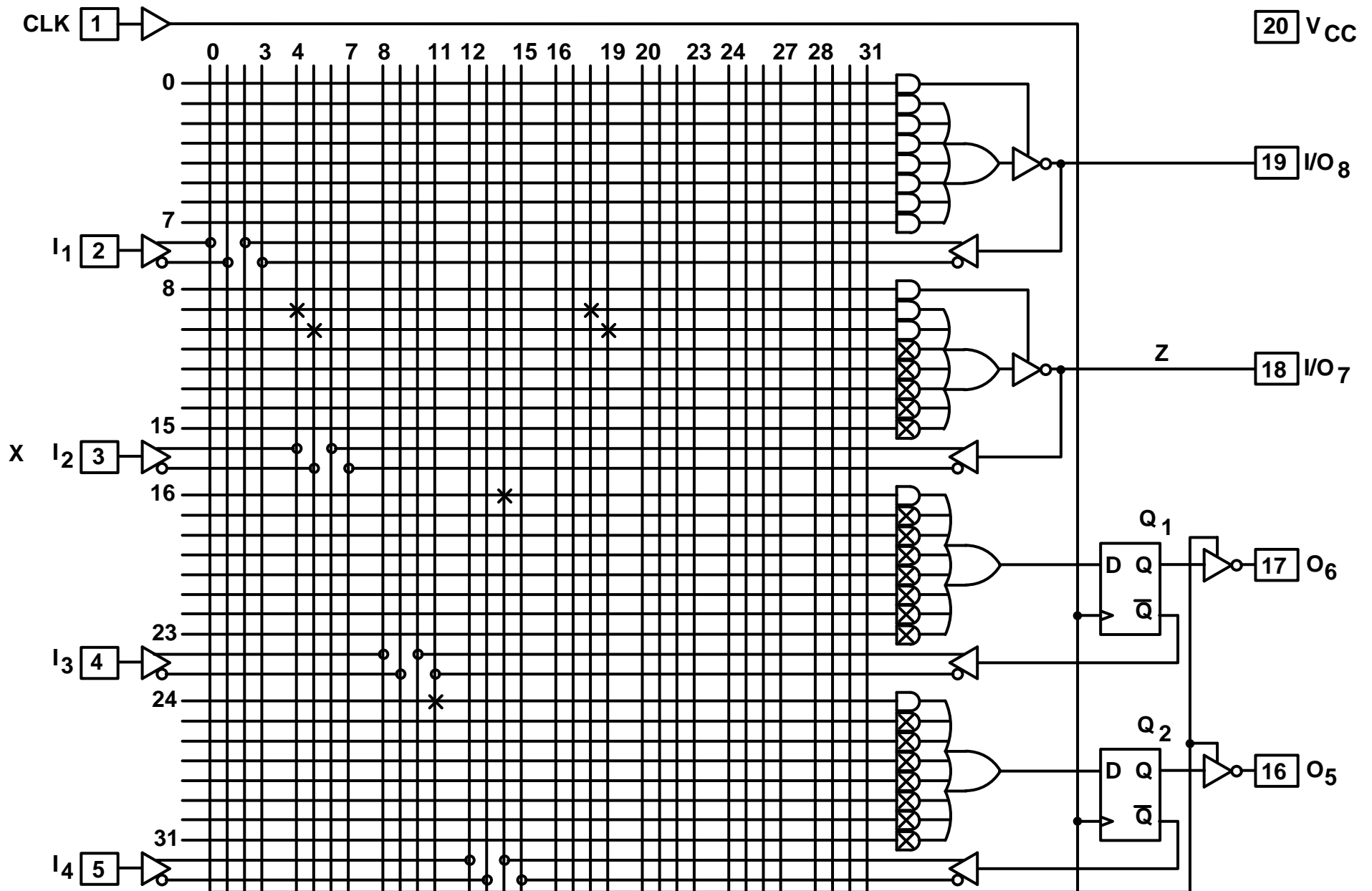


Figure 3-14b Logic Diagram for 16R4 PAL

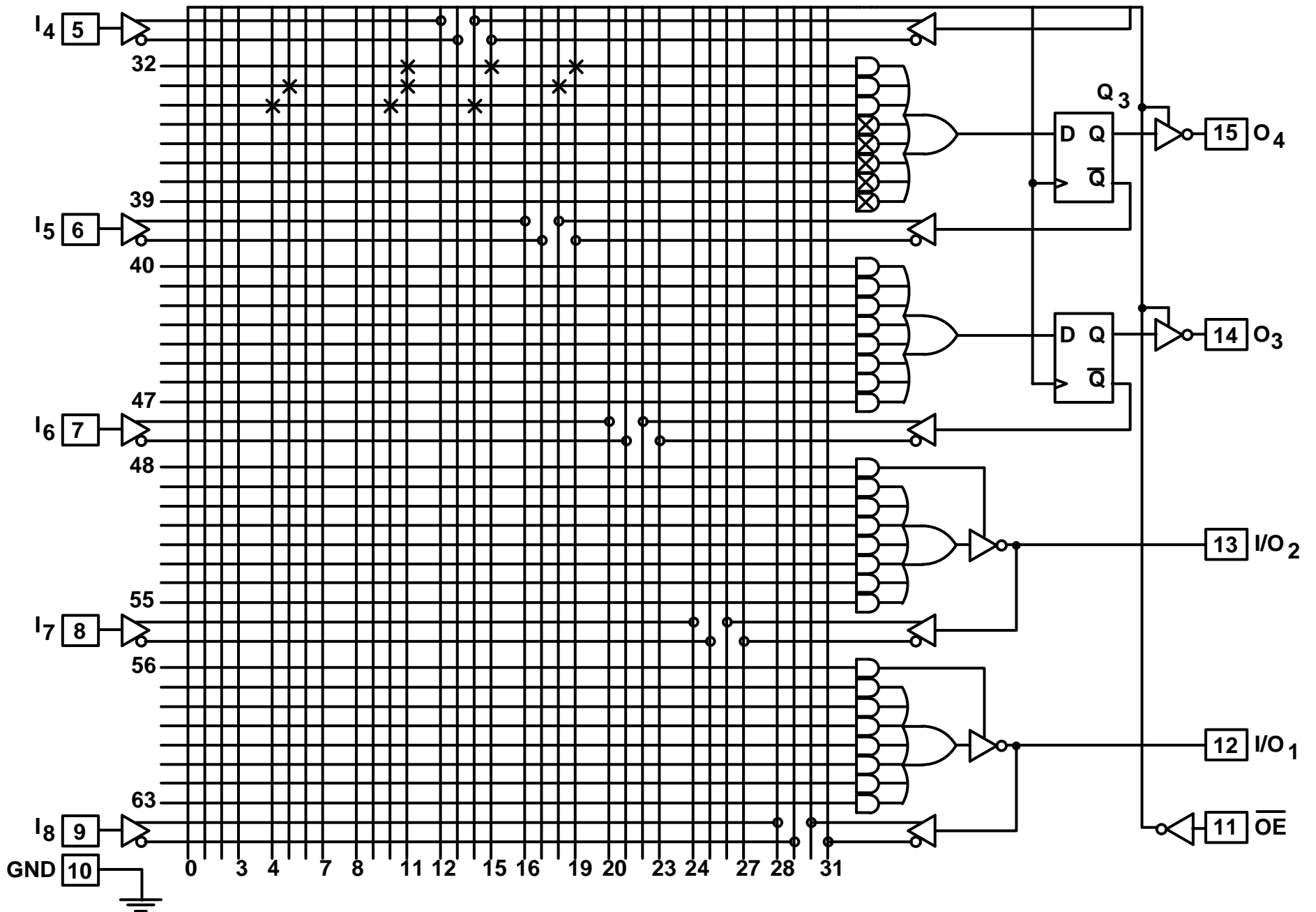


Figure 3-15 Block Diagram for 22V10


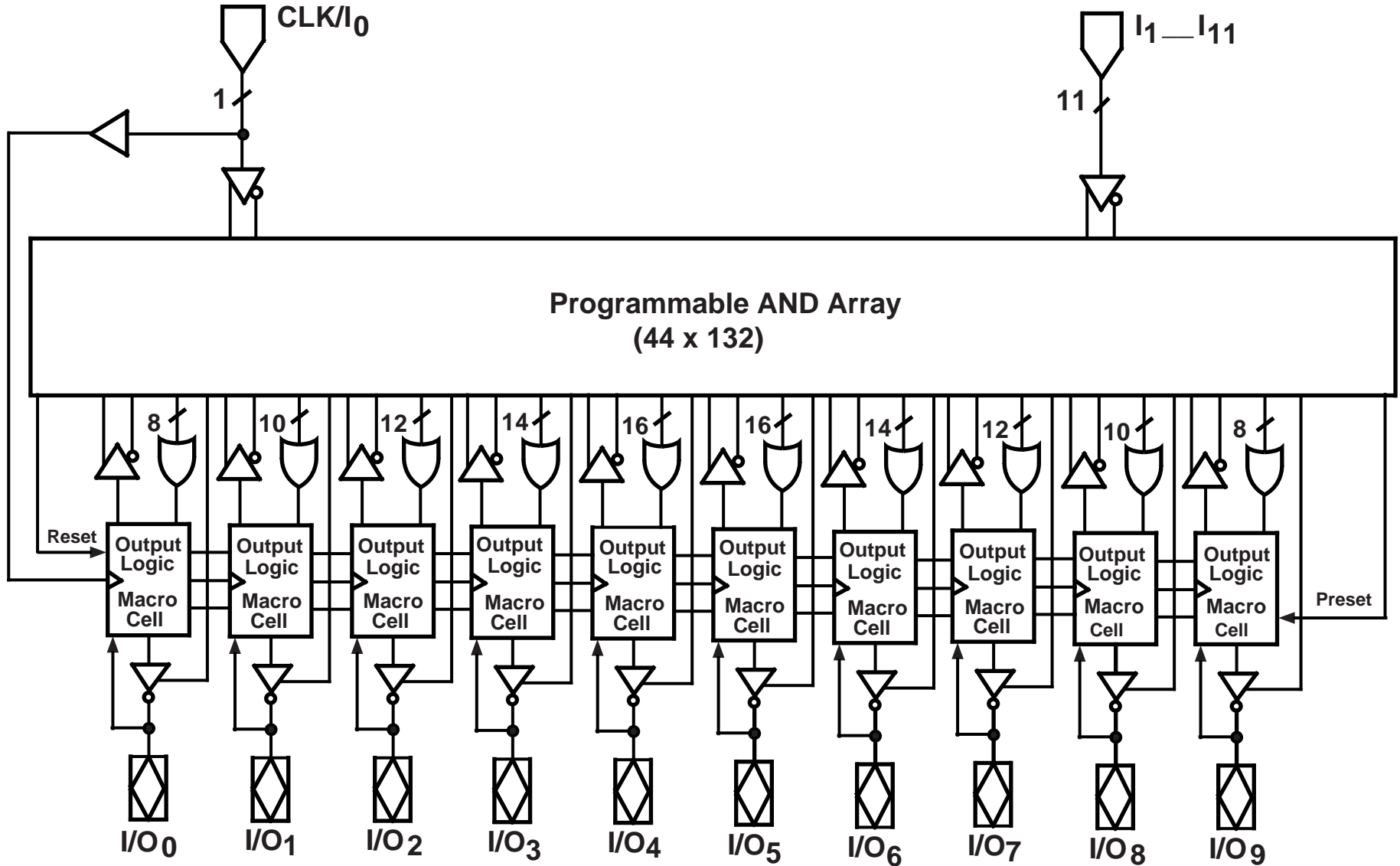


Table 3-5 Characteristics of Simple CMOS PLD's


Type No.	No. of inputs	I/O	Macrocells = FFs	AND gates per OR gate
PALCE16V10	8 + \overline{OE} + Clk	8	8	8
PALCE20V8	14	8	8	8
PALCE22V10	12	10	10	8-16
PALCE24V10	14	10	10	8
PALCE29MA16	5 + Clk	16	16	4-12
CY7C335	12 + \overline{OE} + Clk	12	12 in/12 out	9-19

Figure 3-16a Output Macrocell

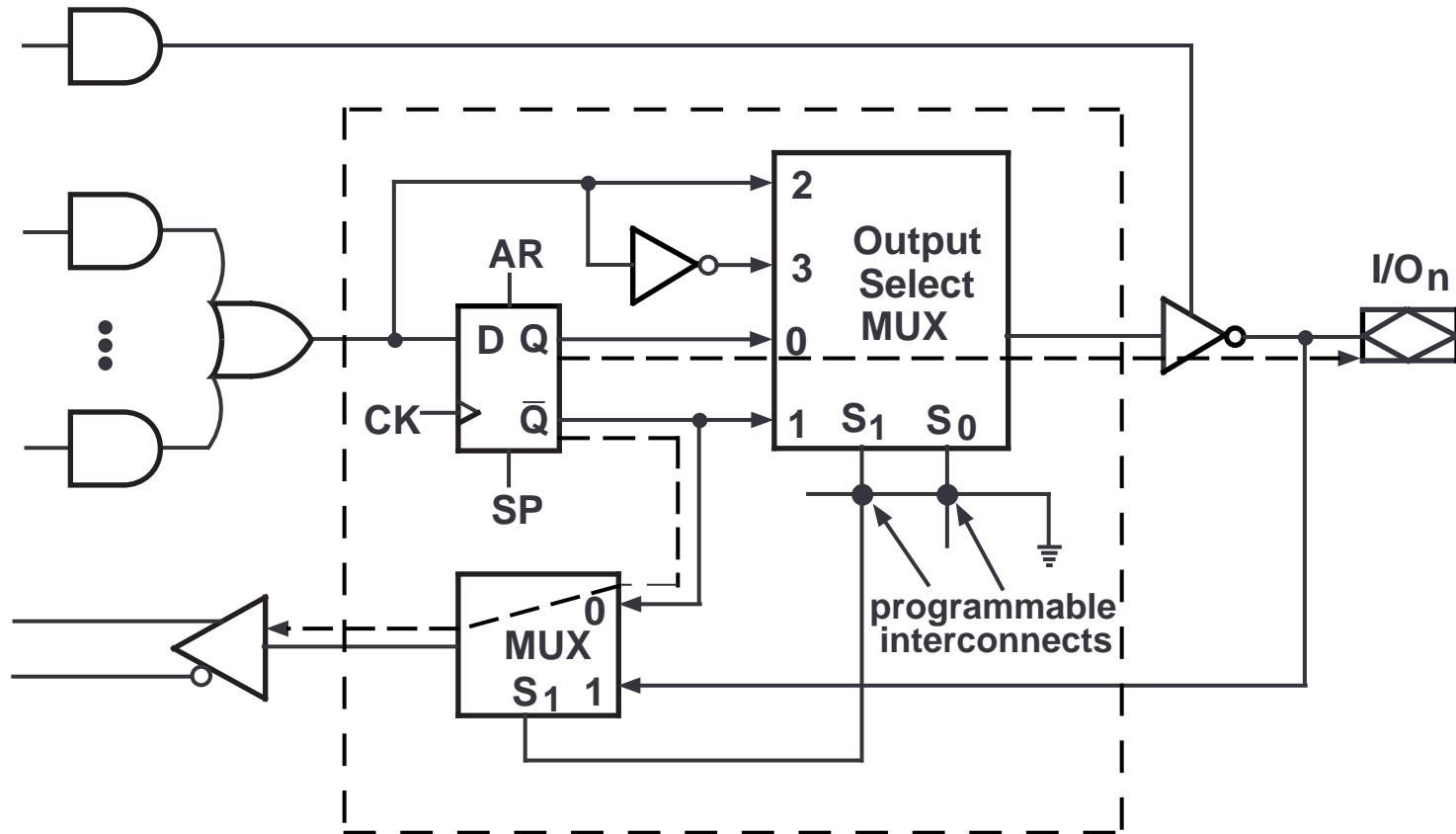

(a) paths with $S_1 = S_0 = 0$

Figure 3-16b Output Macrocell

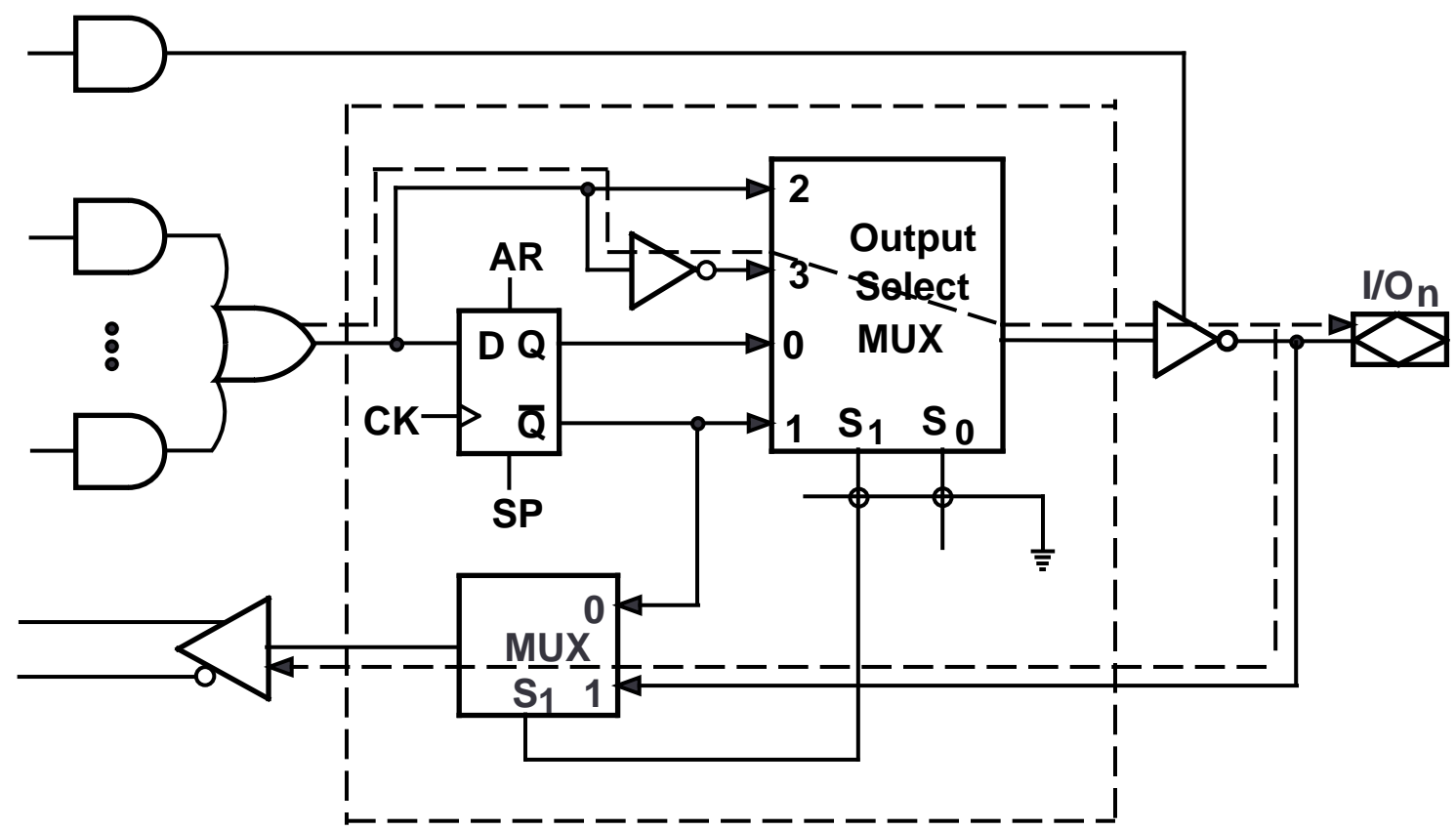

(b) paths with $S_1 = S_0 = 1$

Figure 3-17 Block Diagram of Traffic-Light Controller

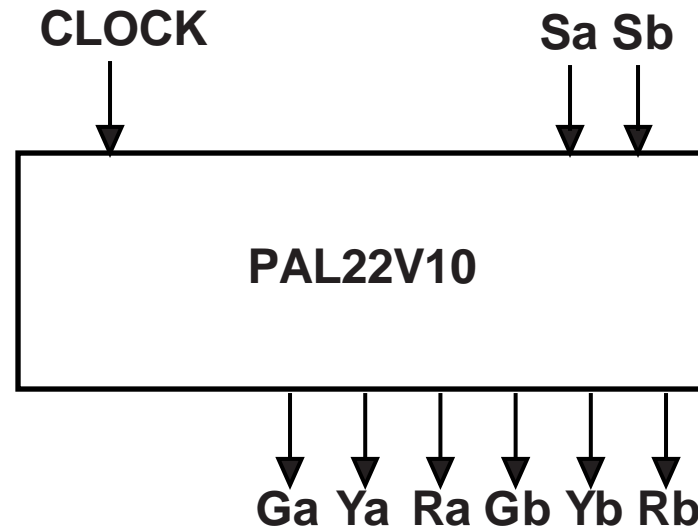


Figure 3-18 State Graph for Traffic-Light Controller

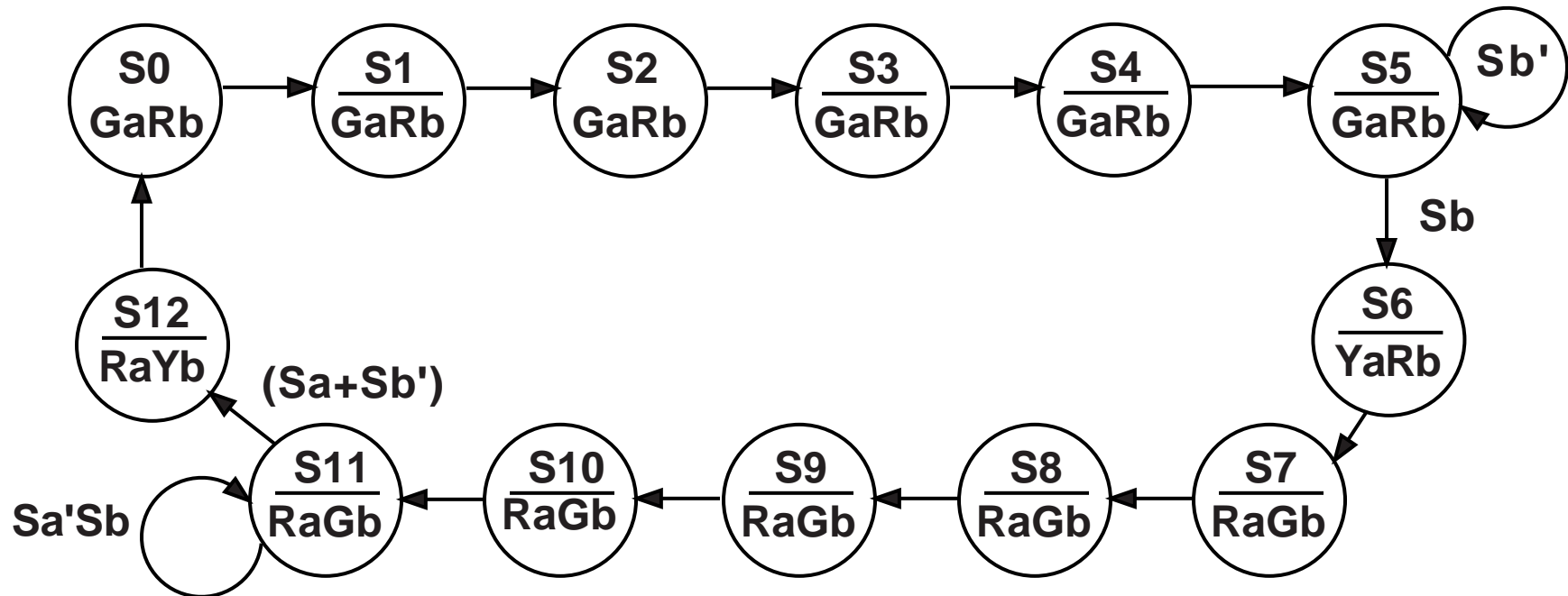


Figure 3-19 VHDL Code for Traffic-Light Controller

```
entity traffic_light is
    port (clk, Sa, Sb: in bit;
           Ra, Rb, Ga, Gb, Ya, Yb: inout bit);
end traffic_light;

architecture behave of traffic_light is
    signal state, nextstate: integer range 0 to 12; type light is (R, Y, G);
    signal lightA, lightB: light;                -- define signals for waveform output
begin
    process(state, Sa, Sb)
    begin
        Ra <= '0'; Rb <= '0'; Ga <= '0'; Gb <= '0'; Ya <= '0'; Yb <= '0';
        case state is
            when 0 to 4 => Ga <= '1'; Rb <= '1'; nextstate <= state+1;
            when 5 => Ga <= '1'; Rb <= '1'; if Sb = '1' then nextstate <= 6; end if;
            when 6 => Ya <= '1'; Rb <= '1'; nextstate <= 7;
            when 7 to 10 => Ra <= '1'; Gb <= '1'; nextstate <= state+1;
            when 11 => Ra <= '1'; Gb <= '1';
                        if (Sa='1' or Sb='0') then nextstate <= 12; end if;
            when 12 => Ra <= '1'; Yb <= '1'; nextstate <= 0;
        end case;
    end process;
    process(clk)
    begin
        if clk = '1' then state <= nextstate; end if;
    end process;
    lightA <= R when Ra='1' else Y when Ya='1' else G when Ga='1';
    lightB <= R when Rb='1' else Y when Yb='1' else G when Gb='1';
end behave;
```

Figure 3-20 Test Results for Traffic-Light Controller

```

wave clk SA SB state lightA lightB
force clk 0 0,1 5 sec -repeat 10 sec
force SA 1 0, 0 40, 1 170, 0 230, 1 250 sec
force SB 0 0, 1 70, 0, 100, 1 120, 0 150, 1 210, 0 250, 1 270 sec
    
```

 


Table 3-6 State Table for Traffic-Light Controller

	<i>SaSb</i>				<i>Ga</i>	<i>Ya</i>	<i>Ra</i>	<i>Gb</i>	<i>Yb</i>	<i>Rb</i>	
	00	01	10	11							
S0	S1	S1	S1	S1	1	0	0	0	0	1	{Green A, Red B}
S1	S2	S2	S2	S2	1	0	0	0	0	1	
S2	S3	S3	S3	S3	1	0	0	0	0	1	
S3	S4	S4	S4	S4	1	0	0	0	0	1	
S4	S5	S5	S5	S5	1	0	0	0	0	1	
S5	S5	S6	S5	S6	1	0	0	0	0	1	
S6	S7	S7	S7	S7	0	1	0	0	0	1	{Ya,Rb}
S7	S8	S8	S8	S8	0	0	1	1	0	0	{Ra,Gb}
S8	S9	S9	S9	S9	0	0	1	1	0	0	
S9	S10	S10	S10	S10	0	0	1	1	0	0	
S10	S11	S11	S11	S11	0	0	1	1	0	0	
S11	S12	S11	S12	S12	0	0	1	1	0	0	
S12	S0	S0	S0	S0	0	0	1	0	1	0	{Ra,Yb}

$$D1 = Q1 Q2' + Q2 Q3 Q4$$

$$D2 = Q1'Q2'Q3 Q4 + Sa Q1 Q3 Q4 + Sb'Q1 Q3 Q4 + Q1'Q2 Q4' + Q1'Q2 Q3'$$


$$D3 = Q3 Q4' + Sb Q3'Q4 + Q2'Q3'Q4 + Sa'Sb Q1 Q4$$

$$D4 = Sa'Sb Q1 Q3 + Q2'Q4' + Q1'Q4' + Sa Sb'Q2 Q3'Q4$$

$$Ga = Q1' Q3' + Q1'Q2' \quad Ya = Q2Q3Q4' \quad Ra = Q1 + Q2Q3Q4$$

$$Gb = Q1 Q2' + Q2Q3Q4 \quad Yb = Q1 Q2 \quad Rb = Q1'Q2' + Q1'Q4' + Q1'Q3'$$

Figure 3-21 Parallel Adder with Accumulator

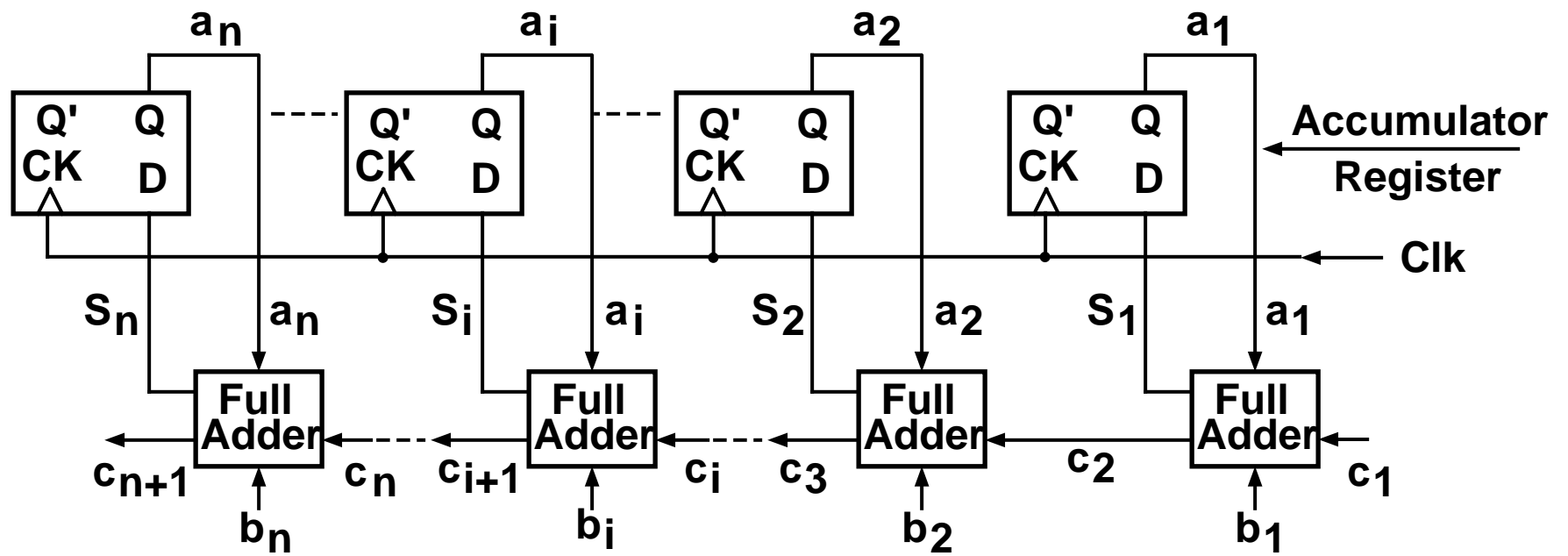

From Page 109

A ₂	A ₁	B ₂	B ₁	C ₁	C ₃	S ₂	S ₁
0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	1
0	0	0	1	0	0	0	1
0	0	0	1	1	0	1	0
0	0	1	0	0	0	1	0
-	-	-	-	-	-	-	-
1	1	0	1	0	1	0	0
1	1	0	1	1	1	0	1
1	1	1	0	0	1	0	1
1	1	1	0	1	1	1	0
1	1	1	1	0	1	1	0
1	1	1	1	1	1	1	1

$$C_3 = B_1 B_2 C_1 + A_1 B_2 C_1 + A_1 B_2 B_1 + A_2 B_1 C_1 + A_2 B_2 + A_1 A_2 C_1 + A_1 A_2 B_1 + A_1 A_2 C_1 + A_1 A_2 B_1$$

$$S_2 = (A_2' B_1 B_2' C_1 + A_1' A_2' B_1' B_2 + A_1' A_2' B_2 C_1' + A_1 A_2' B_2' C_1 + A_1 A_2' B_1 B_2' + A_2' B_1' B_2 C_1' + A_1' A_2 B_1' B_2' + A_1' A_2 B_2' C_1' + A_2 B_1 B_2 C_1 + A_2 B_1' B_2' C_1' + A_1 A_2 B_2 C_1 + A_1 A_2 B_1 B_2) Ad + Ad' A_2$$

$$S_1 = (A_1' B_1' C_1 + A_1' B_1 C_1' + A_1 B_1' C_1' + A_1 B_1 C_1) Ad + Ad' A_1$$

Figure 3-22 Block Diagram for Keypad Scanner

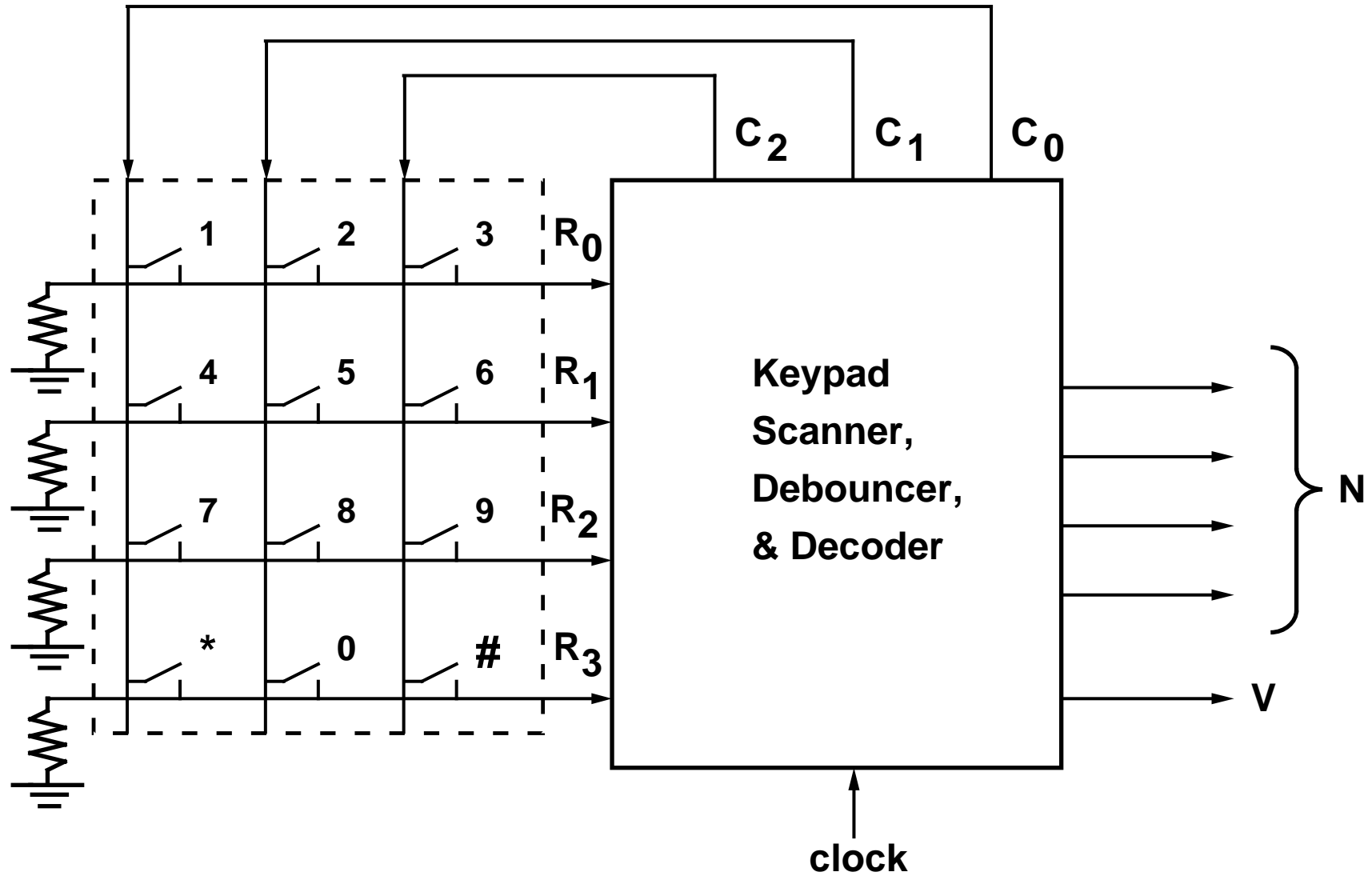


Figure 3-23 Debouncing and Synchronizing Circuit

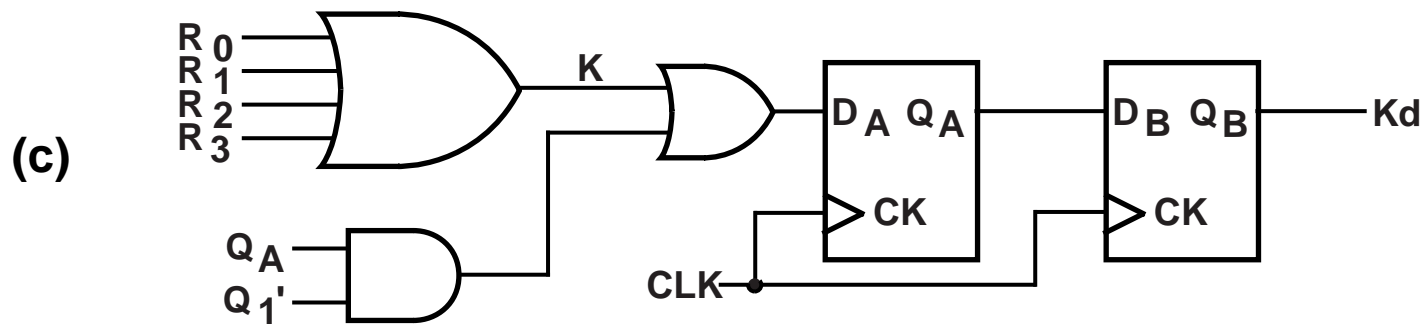
 
 


Figure 3-24 Scanner Modules


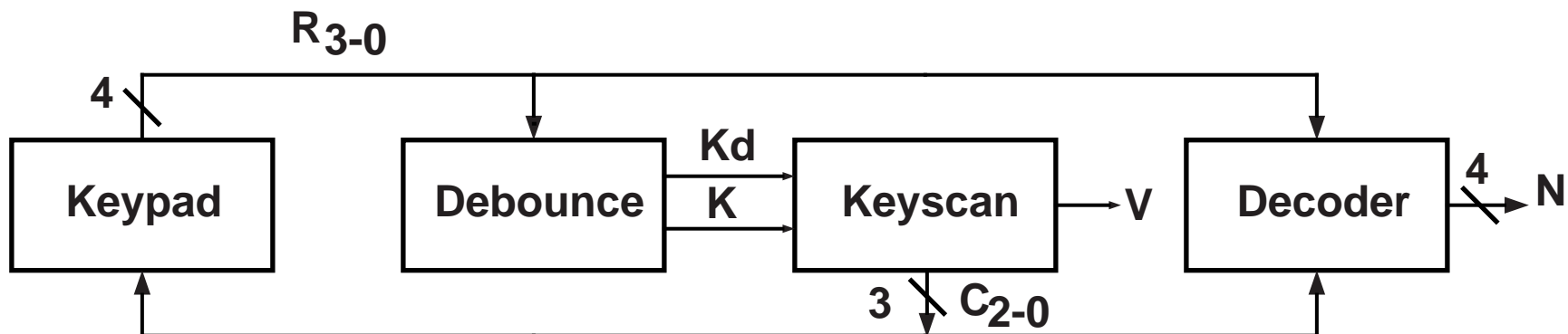


Figure 3-25 State Graph for Scanner

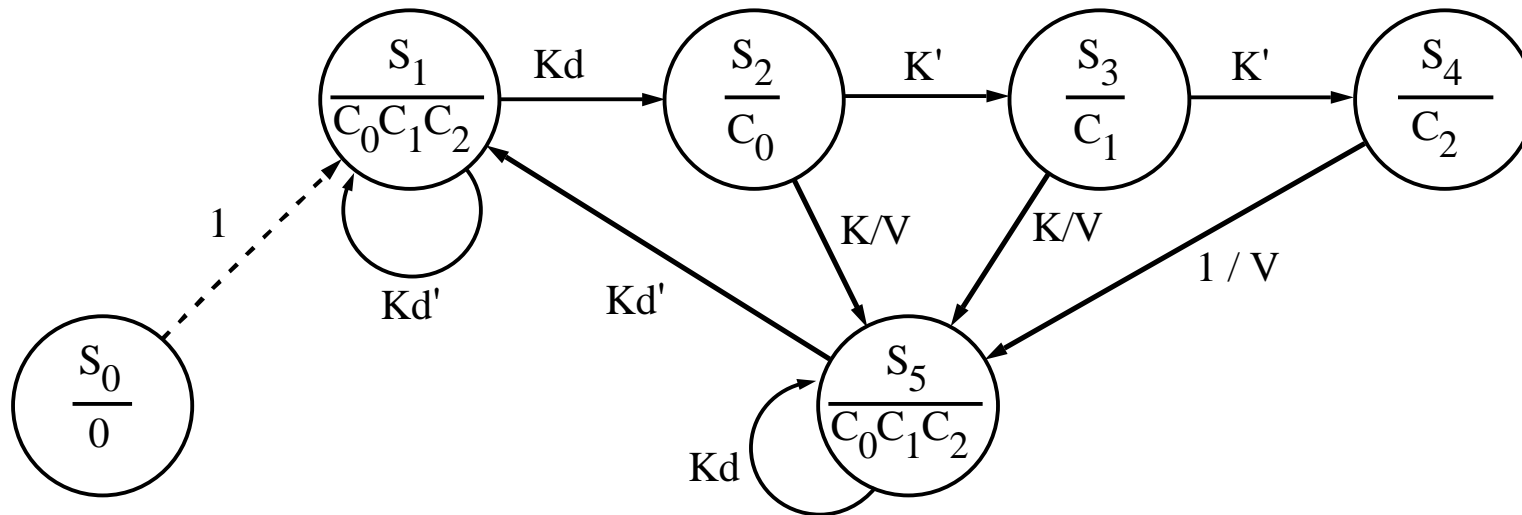

State Assignment for Q1 Q2 Q3 Q4:

$S_1 \leftarrow 0111, S_2 \leftarrow 0100, S_3 \leftarrow 0010, S_4 \leftarrow 0001, S_5 \leftarrow 1111$

$$Q1^+ = Q1 Kd + Q2 Q3'K + Q2'Q3 K + Q2'Q4$$


$$Q2^+ = Q2'Q3' + K + Q4$$

$$Q3^+ = Q3' + Q1 + Q4 Kd' + Q2'K$$

$$Q4^+ = Q2' + Q1 + Q3 Kd' + Q3'K$$

$$V = KQ2Q3' + KQ2'Q3 + Q2'Q4$$

Table 3-7 Truth Table for Decoder

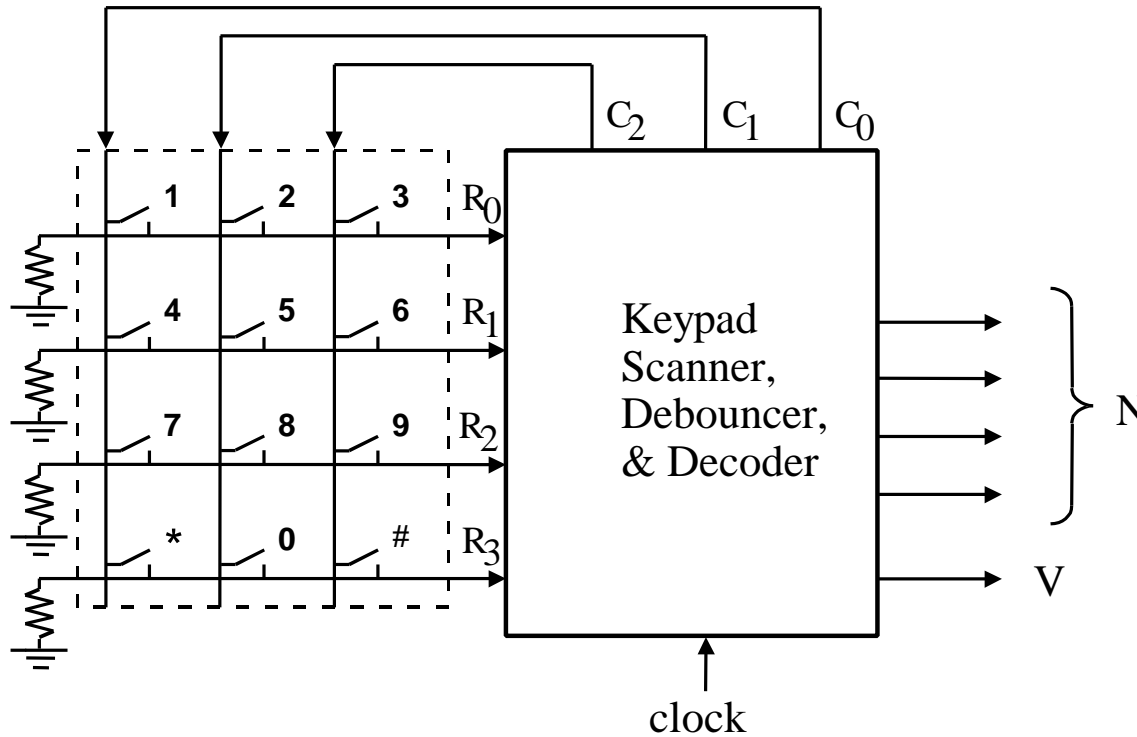

$R_3R_2R_1R_0C_0C_1C_2$	N_3	N_2	N_1	N_0
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

Logic equations for decoder:

$$N_3 = R_2 C_0' + R_3 C_1'$$

$$N_2 = R_1 + R_2 C_0$$

$$N_1 = R_0 C_0' + R_2' C_2 + R_1' R_0' C_0$$

$$N_0 = R_1 C_1 + R_1' C_2 + R_3' R_1' C_1'$$

Figure 3-26 VHDL Code for Scanner

```
entity scanner is
  port (R0,R1,R2,R3,CLK: in bit;
         C0,C1,C2: inout bit;
         N0,N1,N2,N3,V: out bit);
end scanner;
architecture scan1 of scanner is
  signal Q1,QA, K, Kd: bit;
  alias Q2: bit is C0;           -- column outputs will be the same
  alias Q3: bit is C1;           -- as the state variables because
  alias Q4: bit is C2;           -- of state assignment
begin
  K <= R0 or R1 or R2 or R3;      -- this is the decoder section
  N3 <= (R2 and not C0) or (R3 and not C1); N2 <= R1 or (R2 and C0);
  N1 <= (R0 and not C0) or (not R2 and C2) or (not R1 and not R0 and C0);
  N0 <= (R1 and C1) or (not R1 and C2) or (not R3 and not R1 and not C1);
  V <= (Q2 and not Q3 and K) or (not Q2 and Q3 and K) or (not Q2 and Q4);
  process(CLK)                    -- process to update flip-flops
  begin
    if CLK = '1' then
      Q1 <= (Q1 and Kd) or (Q2 and not Q3 and K) or (not Q2 and Q3 and K)
          or (not Q2 and Q4);
      Q2 <= (not Q2 and not Q3) or K or Q4;
      Q3 <= not Q3 or Q1 or (Q4 and not Kd) or (not Q2 and K);
      Q4 <= not Q2 or Q1 or (Q3 and not Kd) or (not Q3 and K);
      QA <= K or (QA and not Q1);      -- first debounce flip-flop
      Kd <= QA;                          -- second debounce flip-flop
    end if;
  end process;
end scan1;
```


Figure 3-27 Interface for Scantest

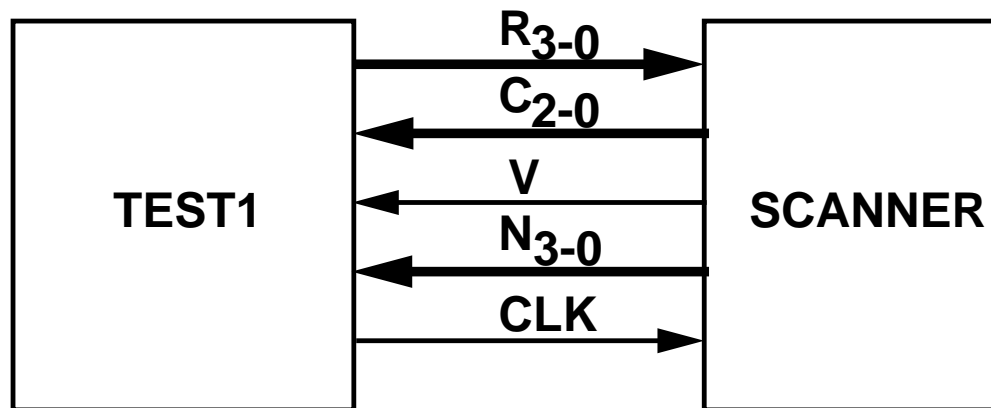


Figure 3-28(a) VHDL for Scantest

```
library BITLIB;
use BITLIB.bit_pack.all;

entity scantest is
end scantest;

architecture test1 of scantest is
component scanner
    port (R0,R1,R2,R3,CLK: in bit;
          C0,C1,C2: inout bit;
          N0,N1,N2,N3,V: out bit);
end component;

type arr is array(0 to 11) of integer;           -- array of keys to test
constant KARRAY:arr := (2,5,8,0,3,6,9,11,1,4,7,10);
signal C0,C1,C2,V,CLK,R0,R1,R2,R3: bit;        -- interface signals
signal N: bit_vector(3 downto 0);
signal KN: integer;                             -- key number to test
begin
    CLK <= not CLK after 20 ns;                  -- generate clock signal
                                                    -- this section emulates the keypad
    R0 <= '1' when (C0='1' and KN=1) or (C1='1' and KN=2) or (C2='1' and KN=3)
    else '0';
    R1 <= '1' when (C0='1' and KN=4) or (C1='1' and KN=5) or (C2='1' and KN=6)
    else '0';
    R2 <= '1' when (C0='1' and KN=7) or (C1='1' and KN=8) or (C2='1' and KN=9)
    else '0';
    R3 <= '1' when (C0='1' and KN=10) or (C1='1' and KN=0) or (C2='1' and KN=11)
    else '0';
```

Figure 3-28(b) VHDL for Scantest

```
process                                     -- this section tests scanner
begin
    for i in 0 to 11 loop                   -- test every number in key array
        KN <= KARRAY(i);                   -- simulates keypress
        wait until (V='1' and rising_edge(CLK));
        assert (vec2int(N) = KN)           -- check if output matches
            report "Numbers don't match"
            severity error;
        KN <= 15;                           -- equivalent to no key pressed
        wait until rising_edge(CLK);       -- wait for scanner to reset
        wait until rising_edge(CLK);
        wait until rising_edge(CLK);
    end loop;
    report "Test complete.";
end process;
scanner1: scanner                           -- connect test1 to scanner
    port map(R0,R1,R2,R3,CLK,C0,C1,C2,N(0),N(1),N(2),N(3),V);
end test1;
```